

EHB436E

DIGITAL SYSTEM DESIGN APPLICATIONS

Muhammed Erkmen
040170049

EXPERIMENT-4 REPORT

Half Adder

Source Code of half adder:

```
`timescale 1ns / 1ps
module arithmetic_circuits(
input x,
input y,
output cout,
output sum
);

HA HA1 (.x(x),.y(y),.sum(sum),.cout(cout));

endmodule

module HA (
input x,
input y,
output cout,
output sum
);
assign sum = ((~x)&&y) || (x&&(~y));
assign cout = x&&y;
endmodule
```

Half adder adds 2 bit and outs sum and cout.

Testbench of half adder:

```

`timescale 1ns / 1ps

module arithmetic_circuits_tb();

reg x;
reg y;
wire sum;
wire cout;
parameter wait_time = 20;
integer i;
// true results

reg [1:0] correct_results_sum[3:0];
reg [1:0] correct_results_cout[3:0];

initial begin
correct_results_sum[0] =0;
correct_results_cout[0] =0 ;
correct_results_sum[1] =1;
correct_results_cout[1] =0 ;
correct_results_sum[2] =1;
correct_results_cout[2] = 0;
correct_results_sum[3] =0;
correct_results_cout[3] = 1;
end

arithmetic_circuits L1 (.x(x),.y(y),.sum(sum),.cout(cout));

initial begin
for (i=0;i<4;i=i+1)
begin
{x,y} = i;
#wait_time;
$write (" {x,y}=%d%d => sum = %d, cout= %d",x,y,sum,cout);
if(sum== correct_results_sum[i] && cout == correct_results_cout[i])
$display(" TRUE");
else
$display(" FALSE");
end
end
endmodule

```

Testbench TCL console output:


```

{x,y}=00 => sum = 0, cout= 0 TRUE
{x,y}=01 => sum = 1, cout= 0 TRUE
{x,y}=10 => sum = 1, cout= 0 TRUE
{x,y}=11 => sum = 0, cout= 1 TRUE


```

I coded true results in testbench, so the outputs show me that everything is okay.


Behavioral simulation of half adder

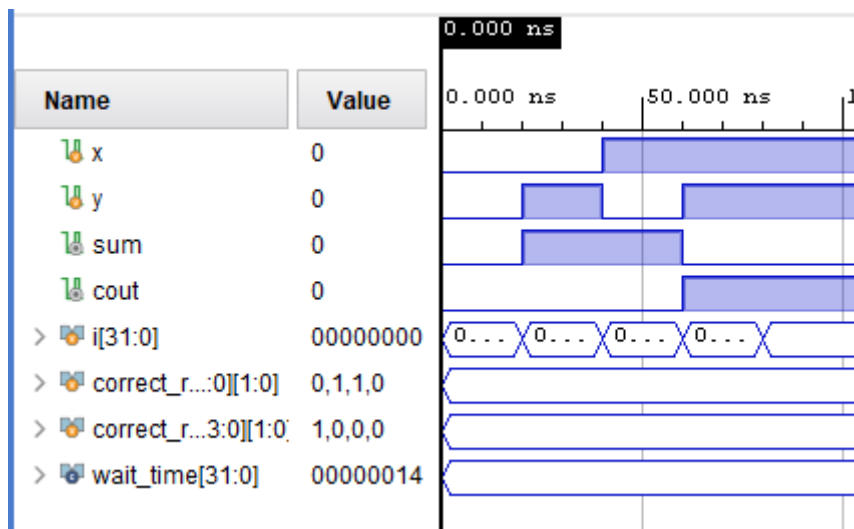

RTL Schematic of half adder

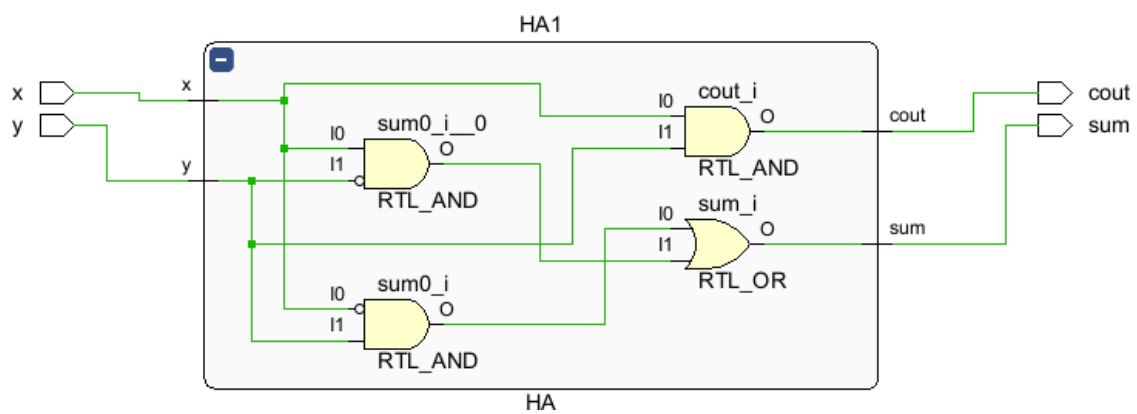

Technology Schematic of half adder

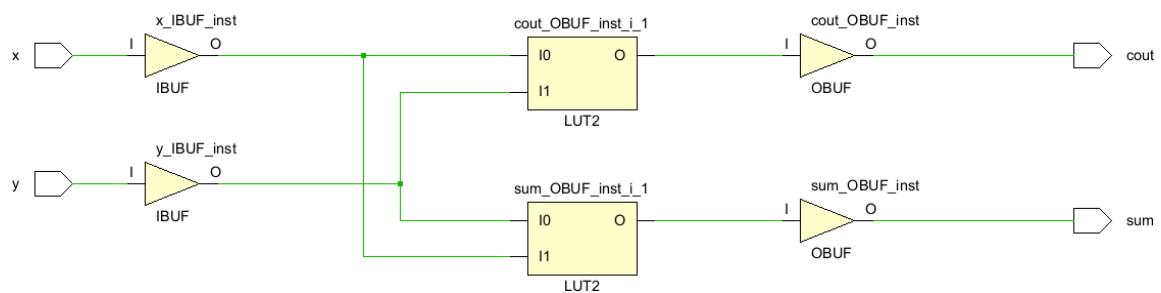


Timing Summary of half adder

| From Port | To Port | M a ¹ | Max Process Corner | Min Delay | Min Process Corner |
|-----------|---------|------------------|--------------------|-----------|--------------------|
| y | cout | 6.983 | SLOW | 2.279 | FAST |
| y | sum | 6.602 | SLOW | 2.184 | FAST |
| x | cout | 6.591 | SLOW | 2.170 | FAST |
| x | sum | 6.242 | SLOW | 2.069 | FAST |

Utilization Report of half adder

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 1 | 32600 | 0.00 |
| IO | 4 | 210 | 1.90 |

 

Only 1 LUT is used in half adder application.

FULL ADDER

Source Code of full adder:

```
`timescale 1ns / 1ps
module arithmetic_circuits(
input x,
input y,
input cin,
output cout,
output sum
);
FA FA1 (.x(x),.y(y),.cin(cin),.sum(sum),.cout(cout));
endmodule

module HA (
input x,
input y,
output cout,
output sum
);
assign sum = ((~x)&&y) || (x&&(~y));
assign cout = x&&y;
endmodule

module FA (
input x,
input y,
input cin,
output cout,
output sum);
wire sum1;
wire cout1;
wire sum2;
wire cout2;

HA HA1 (.x(x),.y(y),.sum(sum1),.cout(cout1));
HA HA2 (.x(sum1),.y(cin),.sum(sum2),.cout(cout2));

assign sum = sum2;
assign cout = cout2 || cout1;

endmodule
```

Full adder adds 2 1-bit number and a carry in.

Testbench of full adder:

```

`timescale 1ns / 1ps
module arithmetic_circuits_tb();
reg x;
reg y;
reg cin;
wire sum;
wire cout;
parameter wait_time = 20;
integer i;
// true results
reg [1:0] correct_results_sum[7:0];
reg [1:0] correct_results_cout[7:0];
initial begin
correct_results_sum[0] = 0;
correct_results_cout[0] = 0 ;
correct_results_sum[1] = 1;
correct_results_cout[1] = 0 ;
correct_results_sum[2] = 1;
correct_results_cout[2] = 0;
correct_results_sum[3] = 0;
correct_results_cout[3] = 1;
//
correct_results_sum[4] = 1;
correct_results_cout[4] = 0 ;
correct_results_sum[5] = 0;
correct_results_cout[5] = 1 ;
correct_results_sum[6] = 0;
correct_results_cout[6] = 1;
correct_results_sum[7] = 1;
correct_results_cout[7] = 1;
end
arithmetic_circuits L1 (.x(x),.y(y),.cin(cin),.sum(sum),.cout(cout));
initial begin
for (i=0;i<8;i=i+1)
begin
{x,y,cin} = i;
#wait_time;
$write (" {x,y,cin}=%d%d%d => sum = %d, cout= %d",x,y,cin,sum,cout);
if(sum== correct_results_sum[i] && cout == correct_results_cout[i])
$display(" TRUE");
else
$display(" FALSE");
end
end
endmodule

```

TCL Console output of full adder:


I coded correct results in testbench so output of testbench shows me everything works fine.

```


Time resolution is 1 ps
{x,y,cin}=000 => sum = 0, cout= 0 TRUE
{x,y,cin}=001 => sum = 1, cout= 0 TRUE
{x,y,cin}=010 => sum = 1, cout= 0 TRUE
{x,y,cin}=011 => sum = 0, cout= 1 TRUE
{x,y,cin}=100 => sum = 1, cout= 0 TRUE
{x,y,cin}=101 => sum = 0, cout= 1 TRUE
{x,y,cin}=110 => sum = 0, cout= 1 TRUE
{x,y,cin}=111 => sum = 1, cout= 1 TRUE

```


Behavioral Simulation of full adder:

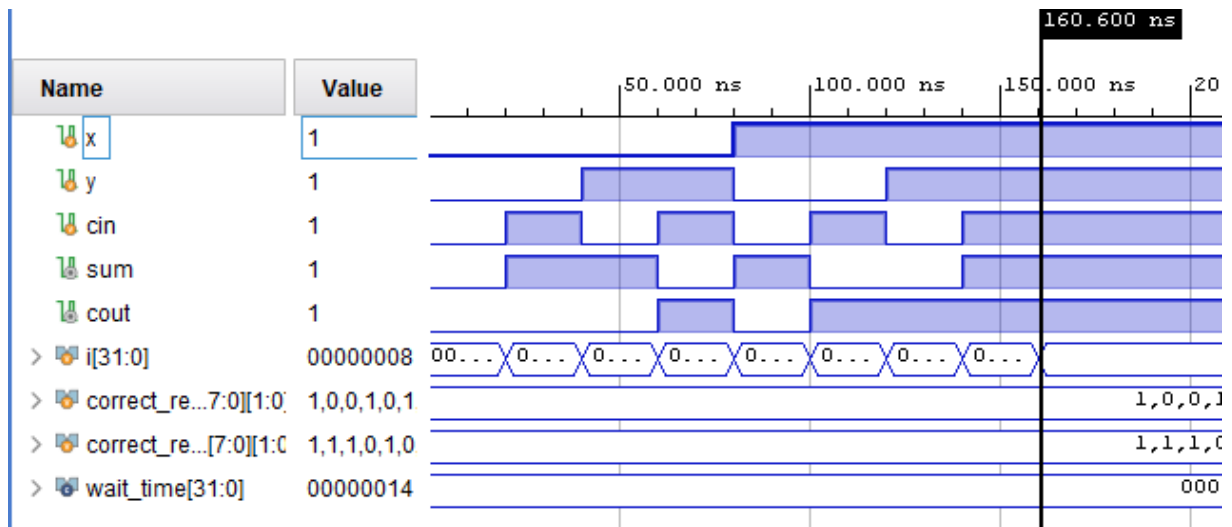

RTL schematic of full adder:

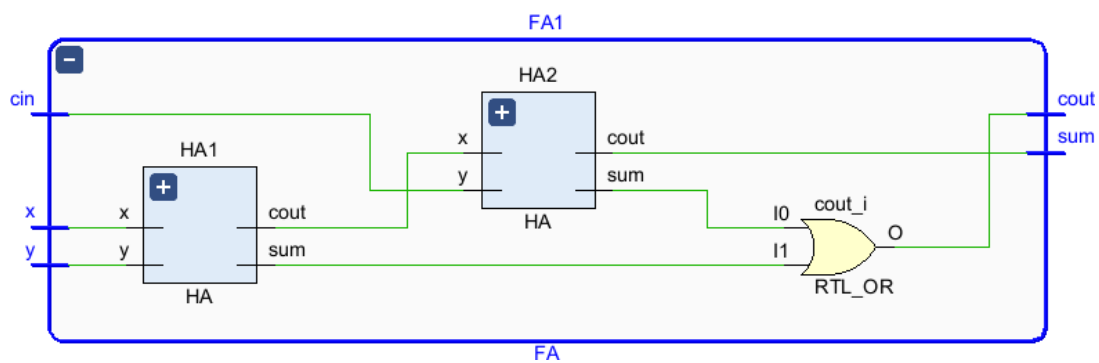


Technology Schematic of full adder:

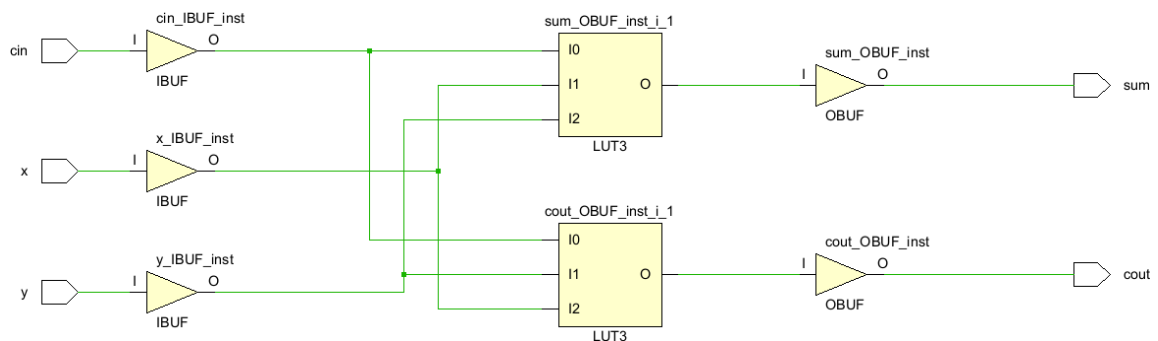


Timing report of full adder:

| Combinational Delays | | | | | |
|----------------------|---------|-----------|--------------------|-----------|--------------------|
| From Port | To Port | Max Delay | Max Process Corner | Min Delay | Min Process Corner |
| x | cout | 6.796 | SLOW | 2.222 | FAST |
| y | cout | 6.726 | SLOW | 2.208 | FAST |
| cin | cout | 6.602 | SLOW | 2.168 | FAST |
| x | sum | 6.541 | SLOW | 2.154 | FAST |
| y | sum | 6.470 | SLOW | 2.145 | FAST |
| cin | sum | 6.379 | SLOW | 2.098 | FAST |

Utilization summary of full adder:

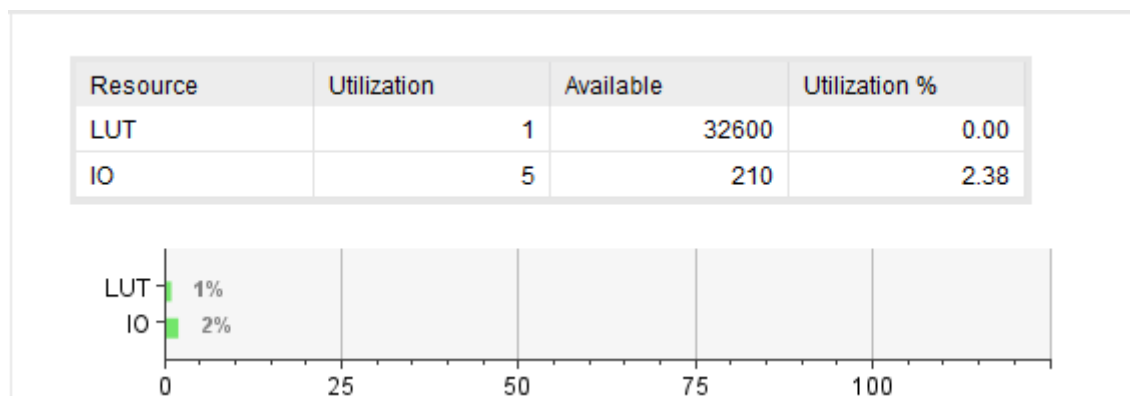

Hand drawing:

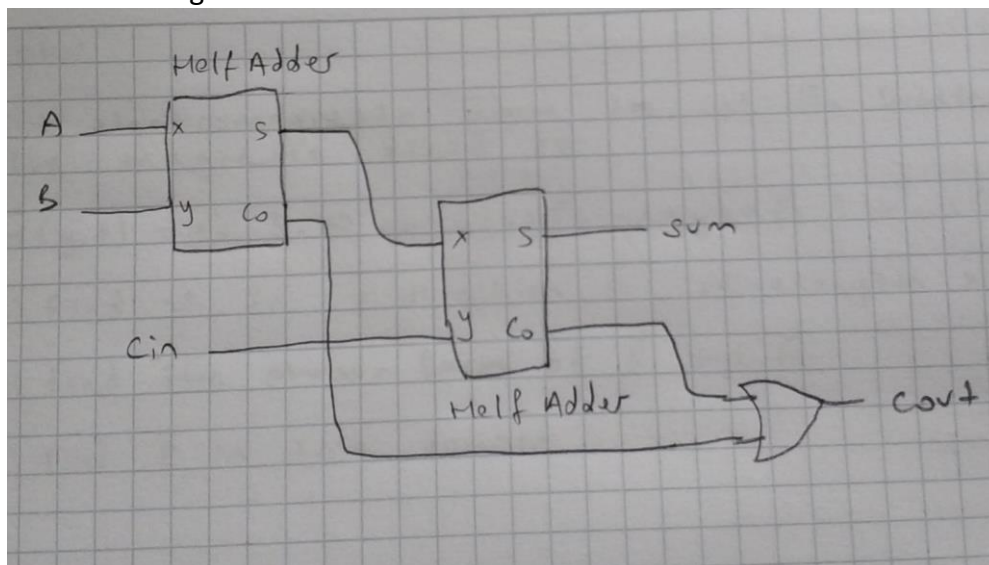

1 LUT used in full adder.

Ripple Carry Adder

This ripple carry adder adds 2 4-bit number with a carry input and outs 4 bit sum and 1 bit carry out.

Source code of ripple carry adder:

```
`timescale 1ns / 1ps
module arithmetic_circuits(
input [3:0] x,
input [3:0] y,
input cin,
output cout,
output [3:0] sum
);
RCA RCA1 (.x(x),.y(y),.cin(cin),.sum(sum),.cout(cout));
endmodule

module HA (
input x,
input y,
output cout,
output sum
);
assign sum = ((~x)&&y) || (x&&(~y));
assign cout = x&&y;
endmodule

module FA (
input x,
input y,
input cin,
output cout,
output sum);
wire sum1;
wire cout1;
wire sum2;
wire cout2;
HA HA1 (.x(x),.y(y),.sum(sum1),.cout(cout1));
HA HA2 (.x(sum1),.y(cin),.sum(sum2),.cout(cout2));
assign sum = sum2;
assign cout = cout2 || cout1;
endmodule

module RCA (
input [3:0] x,
input [3:0] y,
input cin,
output [3:0] sum,
output cout
);
wire cout1,cout2,cout3;
FA FA1 (.x(x[0]),.y(y[0]),.cin(cin),.sum(sum[0]),.cout(cout1));
FA FA2 (.x(x[1]),.y(y[1]),.cin(cout1),.sum(sum[1]),.cout(cout2));
FA FA3 (.x(x[2]),.y(y[2]),.cin(cout2),.sum(sum[2]),.cout(cout3));
FA FA4 (.x(x[3]),.y(y[3]),.cin(cout3),.sum(sum[3]),.cout(cout));
endmodule
```

Testbench of ripple carry adder:

```

`timescale 1ns / 1ps

module arithmetic_circuits_tb();

reg [3:0] x;
reg [3:0] y;
reg cin;
wire [3:0] sum;
wire cout;
parameter wait_time = 10;
integer i;
integer a=0;
// true results

reg [4:0] correct_results[31:0];

initial begin
correct_results[0]= 5'd1 ;
correct_results[1]= 5'd3 ;correct_results[2]= 5'd5 ;
correct_results[3]= 5'd7 ;correct_results[4]= 5'd9 ;
correct_results[5]= 5'd11 ;correct_results[6]= 5'd13 ;
correct_results[7]= 5'd15 ;correct_results[8]= 5'd17 ;
correct_results[9]= 5'd19 ;correct_results[ 10]= 5'd21 ;
correct_results[ 11 ]= 5'd23 ;correct_results[ 12 ]= 5'd25 ;
correct_results[ 13 ]= 5'd27 ;correct_results[ 14 ]= 5'd29 ;
correct_results[ 15 ]= 5'd31 ;

end

arithmetic_circuits L1
(.x(x),.y(y),.cin(cin),.sum(sum),.cout(cout));

initial begin

for (i=0;i<16;i=i+1)
begin
x=i;
y=i;
cin=1;
#wait_time;
$write ("{x,y,cin}=%d%d%d => sum = %d, cout=
%d",x,y,cin,sum,cout);
if({cout,sum} == correct_results[i])
$display(" TRUE");
else
$display(" FALSE");
end

end
endmodule

```

Tcl console output of ripple carry adder:


```

Messages Log Tcl Console x
[Icons]


Compiling module xil_defaultlib.arithmetic_circuits
Compiling module xil_defaultlib.arithmetic_circuits_tb
Compiling module xil_defaultlib.glbl
Built simulation snapshot arithmetic_circuits_tb_behav
INFO: [USF-XSim-69] 'elaborate' step finished in '3' seconds
Time resolution is 1 ps
{x,y,cin}= 0 01 => sum = 1, cout= 0 TRUE
{x,y,cin}= 1 11 => sum = 3, cout= 0 TRUE
{x,y,cin}= 2 21 => sum = 5, cout= 0 TRUE
{x,y,cin}= 3 31 => sum = 7, cout= 0 TRUE
{x,y,cin}= 4 41 => sum = 9, cout= 0 TRUE
{x,y,cin}= 5 51 => sum = 11, cout= 0 TRUE
{x,y,cin}= 6 61 => sum = 13, cout= 0 TRUE
{x,y,cin}= 7 71 => sum = 15, cout= 0 TRUE
{x,y,cin}= 8 81 => sum = 1, cout= 1 TRUE
{x,y,cin}= 9 91 => sum = 3, cout= 1 TRUE
{x,y,cin}=10 101 => sum = 5, cout= 1 TRUE
{x,y,cin}=11 111 => sum = 7, cout= 1 TRUE
{x,y,cin}=12 121 => sum = 9, cout= 1 TRUE
{x,y,cin}=13 131 => sum = 11, cout= 1 TRUE
{x,y,cin}=14 141 => sum = 13, cout= 1 TRUE
{x,y,cin}=15 151 => sum = 15, cout= 1 TRUE
relaunch_sim: Time (s): cpu = 00:00:01 ; elapsed = 00:00:07 . Memory (MB): peak = 2790.633 ; gain = 0.000

```

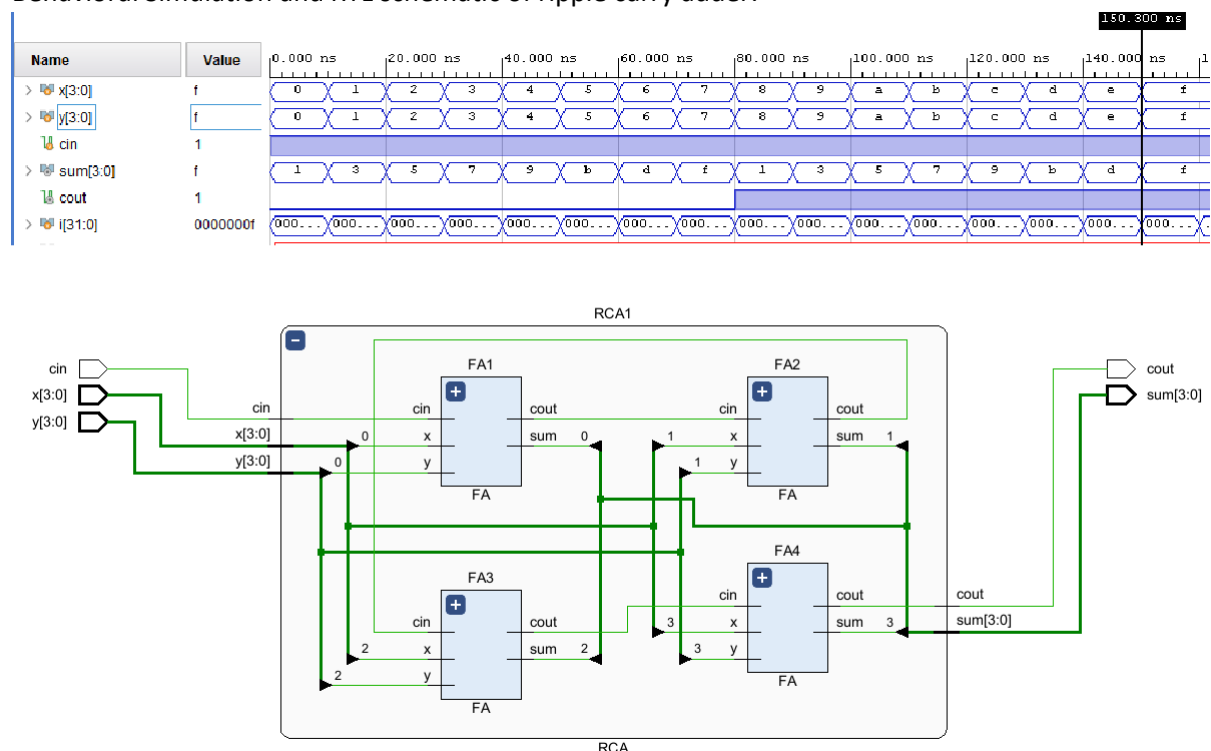Behavioral Simulation and RTL schematic of ripple carry adder:



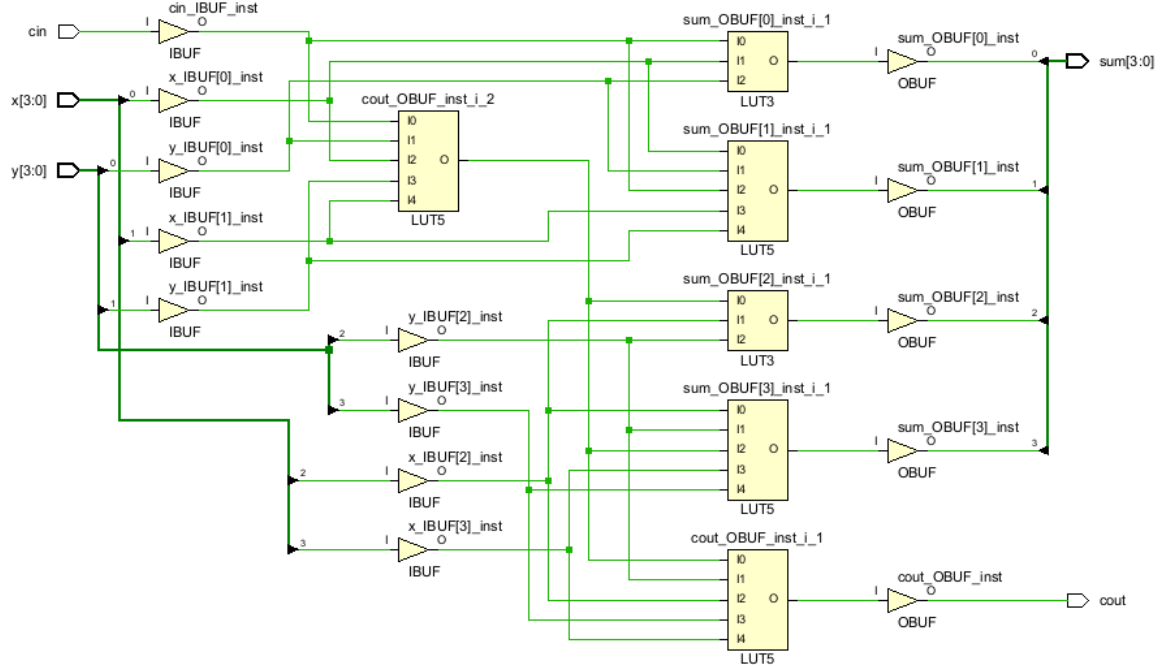Technology schematic of ripple carry adder




Timing report of ripple carry adder:

| Combinational Delays | | | | | |
|----------------------|---------|--------------------|-----------|--------------------|------|
| From Port | To Port | Max Process Corner | Min Delay | Min Process Corner | |
| y[0] | cout | 11.790 | SLOW | 4.204 | FAST |
| x[0] | cout | 11.259 | SLOW | 4.011 | FAST |
| x[1] | cout | 11.187 | SLOW | 3.947 | FAST |
| y[1] | cout | 11.095 | SLOW | 3.926 | FAST |
| cin | cout | 10.865 | SLOW | 3.856 | FAST |
| x[3] | cout | 10.416 | SLOW | 3.710 | FAST |
| y[2] | cout | 10.395 | SLOW | 3.772 | FAST |
| y[0] | sum[2] | 10.312 | SLOW | 3.252 | FAST |
| y[3] | cout | 10.123 | SLOW | 3.562 | FAST |
| y[0] | sum[3] | 10.041 | SLOW | 3.091 | FAST |
| x[2] | cout | 9.893 | SLOW | 3.467 | FAST |
| x[0] | sum[2] | 9.781 | SLOW | 3.059 | FAST |
| x[1] | sum[2] | 9.709 | SLOW | 2.995 | FAST |
| y[1] | sum[2] | 9.617 | SLOW | 2.974 | FAST |
| y[2] | sum[2] | 9.549 | SLOW | 2.998 | FAST |
| x[0] | sum[3] | 9.510 | SLOW | 2.898 | FAST |
| x[1] | sum[3] | 9.438 | SLOW | 2.834 | FAST |
| y[0] | sum[0] | 9.405 | SLOW | 2.887 | FAST |
| cin | sum[2] | 9.387 | SLOW | 2.904 | FAST |
| y[1] | sum[3] | 9.346 | SLOW | 2.813 | FAST |
| y[0] | sum[1] | 9.269 | SLOW | 2.825 | FAST |
| cin | sum[3] | 9.116 | SLOW | 2.742 | FAST |
| x[2] | sum[2] | 9.008 | SLOW | 2.711 | FAST |
| x[0] | sum[1] | 8.736 | SLOW | 2.634 | FAST |
| cin | sum[0] | 8.709 | SLOW | 2.610 | FAST |
| y[2] | sum[3] | 8.680 | SLOW | 2.654 | FAST |
| x[3] | sum[3] | 8.669 | SLOW | 2.599 | FAST |
| x[1] | sum[1] | 8.667 | SLOW | 2.568 | FAST |
| x[0] | sum[0] | 8.596 | SLOW | 2.615 | FAST |
| y[1] | sum[1] | 8.572 | SLOW | 2.545 | FAST |
| y[3] | sum[3] | 8.374 | SLOW | 2.448 | FAST |
| cin | sum[1] | 8.310 | SLOW | 2.481 | FAST |
| x[2] | sum[3] | 8.146 | SLOW | 2.352 | FAST |

Utilization summary of ripple carry adder:

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 4 | 32600 | 0.01 |
| IO | 14 | 210 | 6.67 |

 

4 LUTs used in 4-bit RCA .

PARAMETRIZED RIPPLE CARRY ADDER

Source Code of parametrized ripple carry adder:

```
`timescale 1ns / 1ps
module parametric_RCA
#(parameter SIZE = 8) (
input [(SIZE-1):0] x,
input [(SIZE-1):0] y,
input cin,
output cout,
output [(SIZE-1):0] sum);

genvar i;
wire [(SIZE-1):0] cout_inside;
assign cout = cout_inside[SIZE-1];
generate
for (i=0;i<SIZE;i=i+1)
begin
if(i==0)
FA u0
(.x(x[i]),.y(y[i]),.cin(cin),.sum(sum[i]),.cout(cout_inside[i]));
else
FA u1 (.x(x[i]),.y(y[i]),.cin(cout_inside[i-
1]),.sum(sum[i]),.cout(cout_inside[i]));
end
endgenerate
endmodule

module HA (
input x,
input y,
output cout,
output sum
);
assign sum = ((~x)&&~y) || (x&&~y);
assign cout = x&&y;
endmodule

module FA (
input x,
input y,
input cin,
output cout,
output sum);
wire sum1;
wire cout1;
wire sum2;
wire cout2;
HA HA1 (.x(x),.y(y),.sum(sum1),.cout(cout1));
HA HA2 (.x(sum1),.y(cin),.sum(sum2),.cout(cout2));
assign sum = sum2;
assign cout = cout2 || cout1;
endmodule
```


Testbench Code of parametric ripple carry adder:

```

`timescale 1ns / 1ps

module parametric_RCA_tb;
localparam SIZE = 8;
reg [(SIZE-1):0] x;
reg [(SIZE-1):0] y;
reg cin;
wire cout;
wire [(SIZE-1):0] sum;
wire [SIZE:0] total_sum;


assign total_sum = {cout,sum};

parametric_RCA #(.SIZE(SIZE)) U0
(.x(x),.y(y),.cin(cin),.cout(cout),.sum(sum));

initial begin
x=8'd217;
y=8'd65;
cin=0;
#20;
x=8'd200;
y=8'd150;
cin=0;
#20;
x=8'd110;
y=8'd221;
cin=1;
#20;
x=8'd249;
y=8'd107;
cin=1;
#20;
$finish;
end

```

Simulation Results of parametric RCA:

 


We expect $10+7+1 = 18$ in total sum : {cout,sum} so this case is working true.


We expect $8+14+0=22$ in total sum : {cout,sum} and this case is working true too.

We expect $3+10+0=13$ in total sum {cout,sum} and this case is working true.

RTL Schematic of parametric RCA:

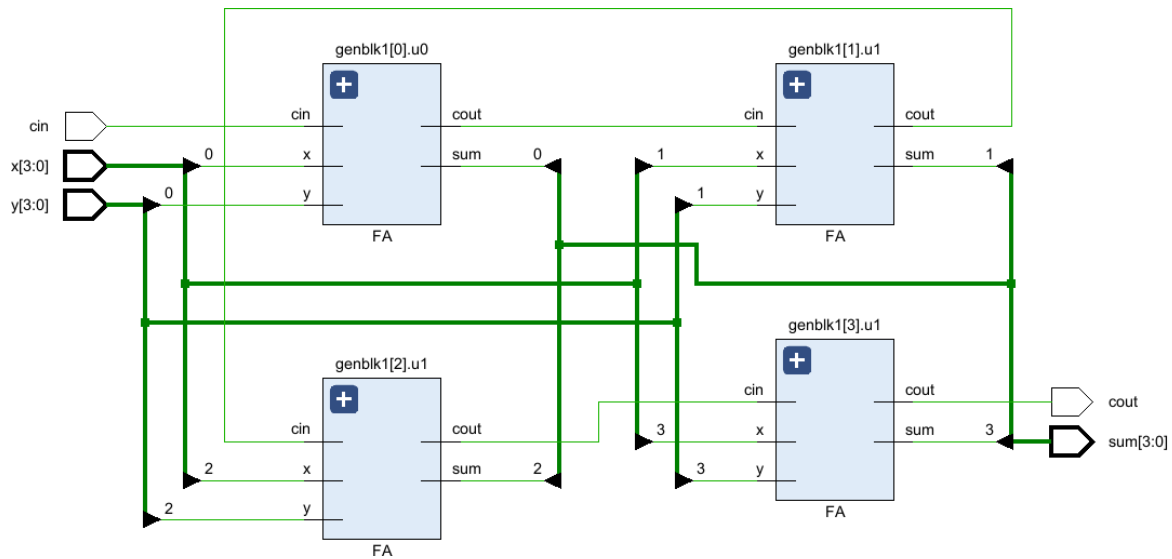

Technology Schematic of parametric RCA:

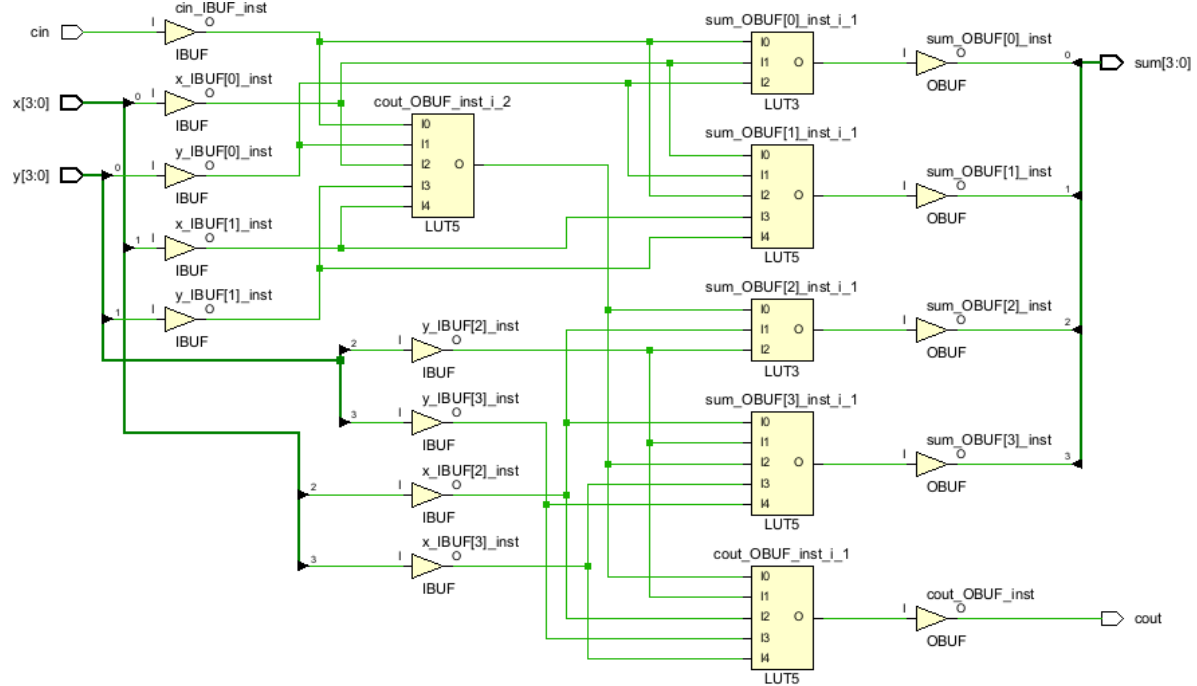


Timing summary of parametric RCA:

| From Port | To Port | Ma ₁ | Max Process Corner | Min Delay | Min Process Corner |
|-----------|---------|-----------------|--------------------|-----------|--------------------|
| y[0] | cout | 11.790 | SLOW | 4.204 | FAST |
| x[0] | cout | 11.259 | SLOW | 4.011 | FAST |
| x[1] | cout | 11.187 | SLOW | 3.947 | FAST |
| y[1] | cout | 11.095 | SLOW | 3.926 | FAST |
| cin | cout | 10.865 | SLOW | 3.856 | FAST |
| x[3] | cout | 10.416 | SLOW | 3.710 | FAST |
| y[2] | cout | 10.395 | SLOW | 3.772 | FAST |
| y[0] | sum[2] | 10.312 | SLOW | 3.252 | FAST |
| y[3] | cout | 10.123 | SLOW | 3.562 | FAST |
| y[0] | sum[3] | 10.041 | SLOW | 3.091 | FAST |
| x[2] | cout | 9.893 | SLOW | 3.467 | FAST |
| x[0] | sum[2] | 9.781 | SLOW | 3.059 | FAST |
| x[1] | sum[2] | 9.709 | SLOW | 2.995 | FAST |
| y[1] | sum[2] | 9.617 | SLOW | 2.974 | FAST |
| y[2] | sum[2] | 9.549 | SLOW | 2.998 | FAST |
| x[0] | sum[3] | 9.510 | SLOW | 2.898 | FAST |
| x[1] | sum[3] | 9.438 | SLOW | 2.834 | FAST |
| y[0] | sum[0] | 9.405 | SLOW | 2.887 | FAST |
| cin | sum[2] | 9.387 | SLOW | 2.904 | FAST |
| y[1] | sum[3] | 9.346 | SLOW | 2.813 | FAST |
| y[0] | sum[1] | 9.269 | SLOW | 2.825 | FAST |
| cin | sum[3] | 9.116 | SLOW | 2.742 | FAST |
| x[2] | sum[2] | 9.008 | SLOW | 2.711 | FAST |
| x[0] | sum[1] | 8.736 | SLOW | 2.634 | FAST |
| cin | sum[0] | 8.709 | SLOW | 2.610 | FAST |
| y[2] | sum[3] | 8.680 | SLOW | 2.654 | FAST |
| x[3] | sum[3] | 8.669 | SLOW | 2.599 | FAST |
| x[1] | sum[1] | 8.667 | SLOW | 2.568 | FAST |
| x[0] | sum[0] | 8.596 | SLOW | 2.615 | FAST |
| y[1] | sum[1] | 8.572 | SLOW | 2.545 | FAST |
| y[3] | sum[3] | 8.374 | SLOW | 2.448 | FAST |
| cin | sum[1] | 8.310 | SLOW | 2.481 | FAST |
| x[2] | sum[3] | 8.146 | SLOW | 2.352 | FAST |

Utilization report of parametric RCA:


Summary

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 4 | 32600 | 0.01 |
| IO | 14 | 210 | 6.67 |

 

4 LUTs used in 4 bit parametric RCA.

SIZE=8

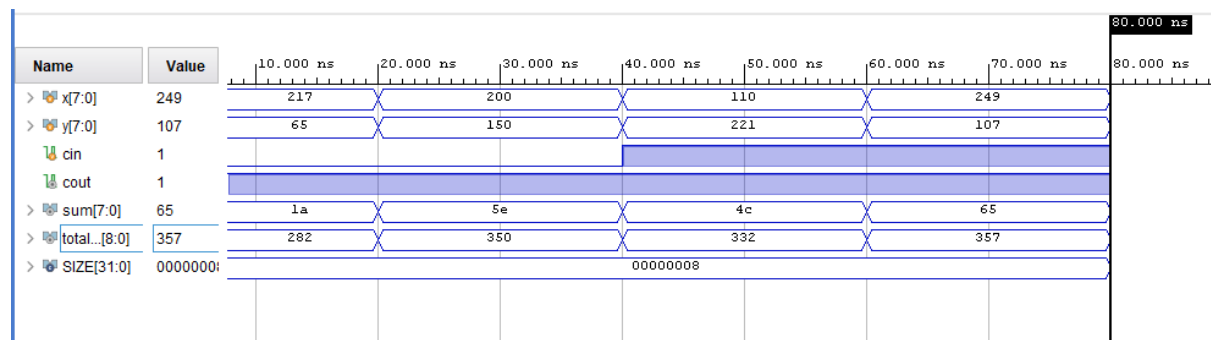

X=249 y=65 and cin=0 we expect 282 in total sum, and that's correct.

x=200 y=150 and cin= 0 , we expect 350 in total sum, and that's correct.

X=110 y=221 and cin=1 = we expect 332 in total sum and that's correct.

Carry lookahead adder:

This is 4-bit inputs and a carry input, carry lookahead adder module.

Source code of carry lookahead adder:

```
`timescale 1ns / 1ps
module CLA(
input [3:0] x,
input [3:0] y,
input cin,
output cout,
output [3:0] sum
);

// P = x^y
// G = x&y
// Digital Design book expressions:
// Si = Pi ^ Ci
// Ci+1 = Gi + PiCi

// C1 = G0 + P0Cin
// C2 = G1 + P1(G0+P0Cin)
// C3 = G2 + P2(G1+(P1(G0+P0Cin)))
// C4 = G3 + P3(G2 + P2(G1+(P1(G0+P0Cin))))
wire [3:0] p,g,c;
assign p = x^y;
assign g = x&y;
assign c[0] = cin;
assign c[1] = g[0] | (p[0]&cin);
assign c[2] = g[1] | (p[1]&(g[0] | (p[0]&cin)));
assign c[3] = g[2] | (p[2]&(g[1] | (p[1]&(g[0] | (p[0]&cin)))));
assign cout = g[3] | (p[3]&(g[2] | (p[2]&(g[1] | (p[1]&(g[0] |
(p[0]&cin)))))));
assign sum = p^c;

endmodule
```

Here $p_i = x_i \oplus y_i$ and $g_i = x_i \cdot y_i$.

And we get carry input values from the $C_{i+1} = G_i + P_i C_i$ formula so that should be faster than ripple carry adder

Testbench Code of carry lookahead adder:

```

`timescale 1ns / 1ps

module CLA_tb;

reg [3:0] x;
reg [3:0] y;
reg cin;
wire cout;
wire [3:0] sum;
wire [4:0] totalsum;
assign totalsum = {cout,sum};


CLA Y1 (.x(x),.y(y),.cin(cin),.cout(cout),.sum(sum));

initial begin

x= 4'd10;
y = 4'd15;
cin = 1;
#20;
x= 4'd11;
y = 4'd14;
cin = 0;
#20;
x= 4'd8;
y = 4'd4;
cin = 0;
#20;
x= 4'd5;
y = 4'd9;
cin = 1;
#20;
$finish;
end
endmodule


```

Simulation Results of CLA:

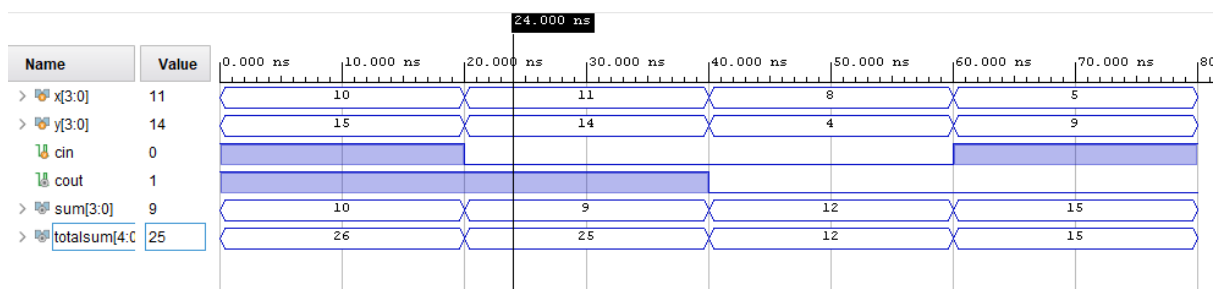


Here is $x = 11$, $y = 14$ and $cin = 0$ so sum should be 25 but it doesn't fit in 4 bits so with cout it becomes 25 as other comes true that way too.

RTL Schematic of CLA:

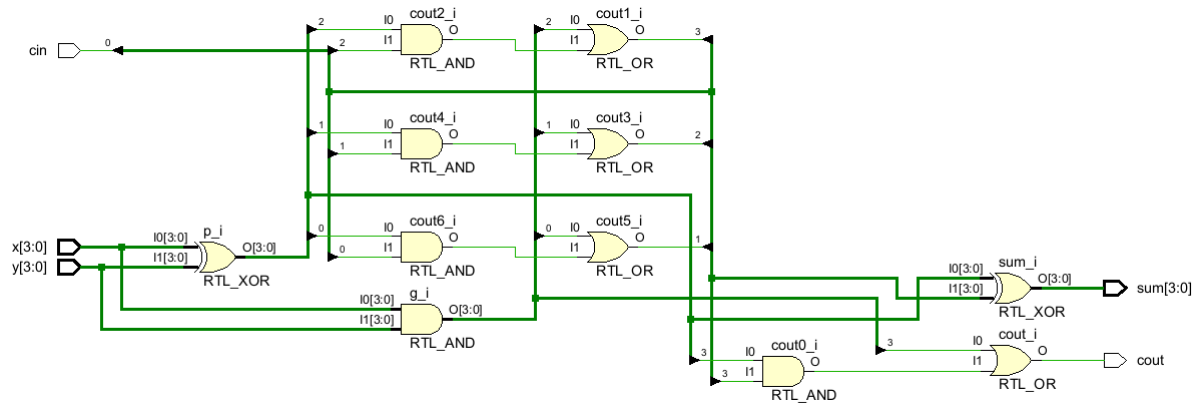


Technology Schematic of CLA:

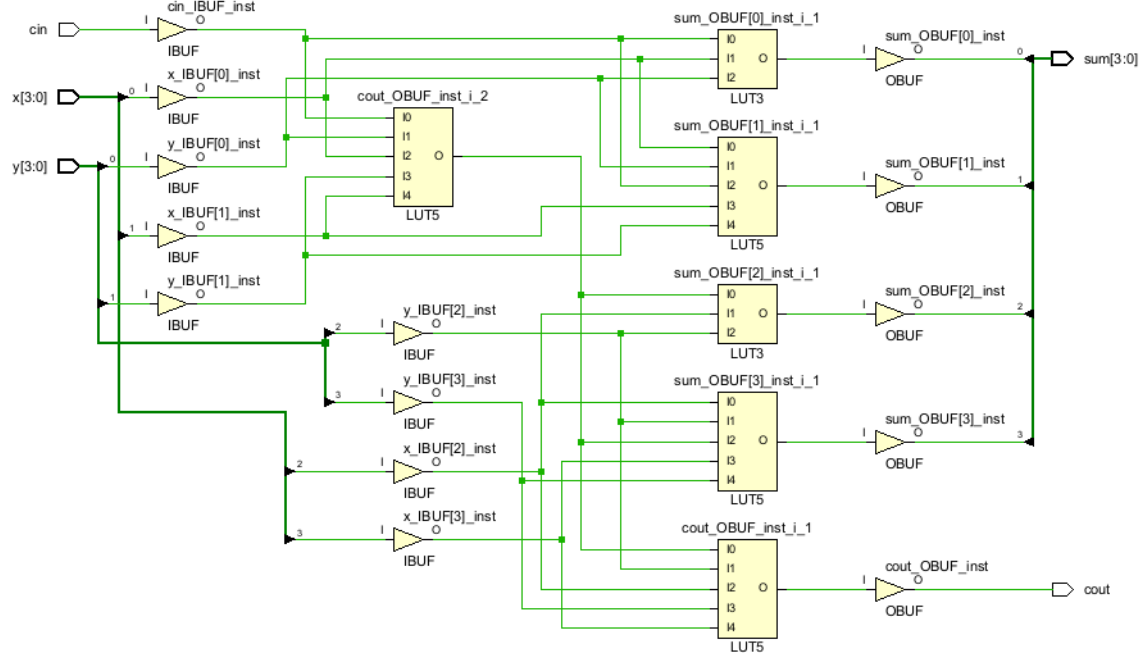


Utilization report of CLA:
Summary

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 4 | 32600 | 0.01 |
| IO | 14 | 210 | 6.67 |

 

Sheet calculations of CLA:

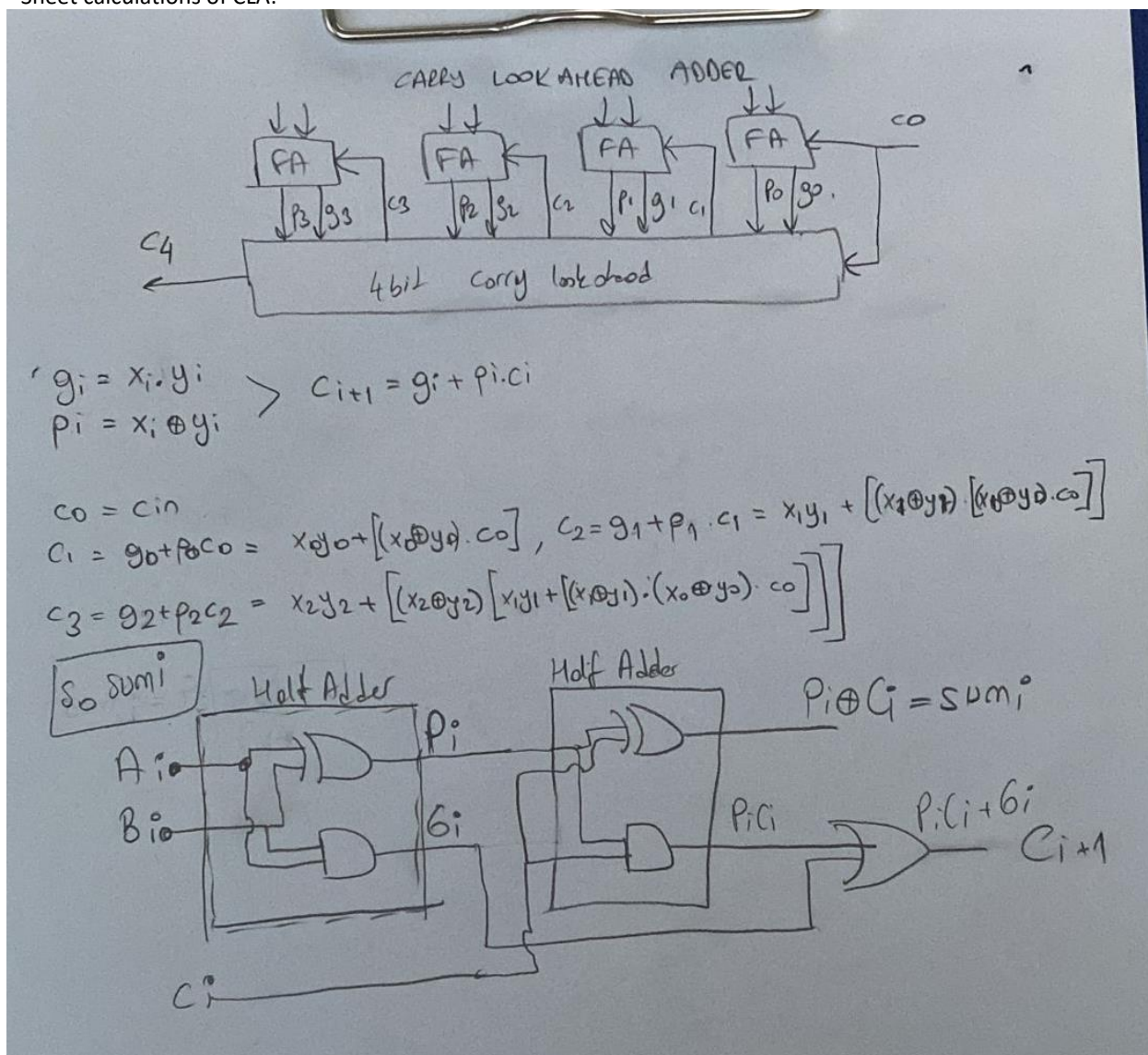

Timing report of CLA:

| From Port | To Port | Max Delay | Max Process Corner | Min Delay | Min Process Corner |
|-----------|---------|-----------|--------------------|-----------|--------------------|
| cin | cout | 11.595 | SLOW | 4.152 | FAST |
| x[0] | cout | 9.246 | SLOW | 2.801 | FAST |
| x[1] | cout | 9.000 | SLOW | 2.706 | FAST |
| x[2] | cout | 8.525 | SLOW | 2.493 | FAST |
| x[3] | cout | 8.818 | SLOW | 2.644 | FAST |
| y[0] | cout | 9.179 | SLOW | 2.778 | FAST |
| y[1] | cout | 8.585 | SLOW | 2.544 | FAST |
| y[2] | cout | 9.459 | SLOW | 2.917 | FAST |
| y[3] | cout | 8.582 | SLOW | 2.507 | FAST |
| cin | sum[0] | 11.445 | SLOW | 4.130 | FAST |
| x[0] | sum[0] | 9.621 | SLOW | 2.966 | FAST |
| y[0] | sum[0] | 9.610 | SLOW | 2.967 | FAST |
| cin | sum[1] | 11.517 | SLOW | 4.116 | FAST |
| x[0] | sum[1] | 9.166 | SLOW | 2.763 | FAST |
| x[1] | sum[1] | 8.922 | SLOW | 2.670 | FAST |
| y[0] | sum[1] | 9.099 | SLOW | 2.744 | FAST |
| y[1] | sum[1] | 8.473 | SLOW | 2.512 | FAST |
| cin | sum[2] | 12.469 | SLOW | 4.489 | FAST |
| x[0] | sum[2] | 10.120 | SLOW | 3.138 | FAST |
| x[1] | sum[2] | 9.875 | SLOW | 3.042 | FAST |
| x[2] | sum[2] | 8.788 | SLOW | 2.648 | FAST |
| y[0] | sum[2] | 10.053 | SLOW | 3.114 | FAST |
| y[1] | sum[2] | 9.459 | SLOW | 2.881 | FAST |
| y[2] | sum[2] | 9.719 | SLOW | 3.071 | FAST |
| cin | sum[3] | 11.266 | SLOW | 4.020 | FAST |
| x[0] | sum[3] | 8.917 | SLOW | 2.669 | FAST |
| x[1] | sum[3] | 8.672 | SLOW | 2.573 | FAST |
| x[2] | sum[3] | 8.166 | SLOW | 2.365 | FAST |
| x[3] | sum[3] | 8.457 | SLOW | 2.517 | FAST |
| y[0] | sum[3] | 8.850 | SLOW | 2.645 | FAST |
| y[1] | sum[3] | 8.256 | SLOW | 2.412 | FAST |
| y[2] | sum[3] | 9.098 | SLOW | 2.791 | FAST |
| y[3] | sum[3] | 8.220 | SLOW | 2.379 | FAST |

As we see last full adder in CLA

x[3] to cout delay is = 8.818 ns

y[3] to cout delay is = 8.582 ns

But in RCA

x[3] to cout delay is = 10.4 ns

y[3] to cout delay is = 10.123 ns

Add-Sub with overflow module

The blank operation is **XOR**.

When cin = 1, it is subtracting.

When cin=0 it is adding.

When output V = 1, the 4 bit sum is not enough. If we put cout as the MSB and get that 5 bit value as the total sum, this value will be correct value of operation. When output V=0, total sum could be wrong so it is enough to take 4 bit sum as a result value of the operation.

Source Code of Add-Sub with overflow:

```
`timescale 1ns / 1ps

module Add_Sub(
input [3:0] x,
input [3:0] y,
input cin,
output cout,
output v,
output [3:0] sum
);

wire [3:0] y_n;
wire [3:0] c_inside;
assign y_n = y^{4{cin}};
assign cout = c_inside[3];
assign v = c_inside[3]^c_inside[2];

FA FA1 (.x(x[0]),.y(y_n[0]),.cin(cin),.cout(c_inside[0]),.sum(sum[0]));
FA FA2 (.x(x[1]),.y(y_n[1]),.cin(c_inside[0]),.cout(c_inside[1]),.sum(sum[1]));
FA FA3 (.x(x[2]),.y(y_n[2]),.cin(c_inside[1]),.cout(c_inside[2]),.sum(sum[2]));
FA FA4 (.x(x[3]),.y(y_n[3]),.cin(c_inside[2]),.cout(c_inside[3]),.sum(sum[3]));

endmodule

module HA (
input x,
input y,
output cout,
output sum
);
assign sum = ((~x)&&y) || (x&&(~y));
assign cout = x&&y;
endmodule

module FA (
input x,
input y,
input cin,
output cout,
output sum);
wire sum1;
wire cout1;
wire sum2;
wire cout2;

HA HA1 (.x(x),.y(y),.sum(sum1),.cout(cout1));
HA HA2 (.x(sum1),.y(cin),.sum(sum2),.cout(cout2));

assign sum = sum2;
assign cout = cout2 || cout1;

endmodule
```

Testbench Code:

```

`timescale 1ns / 1ps
module Add_Sub_tb;

reg [3:0] x=0;
reg [3:0] y=0;
reg cin=0;
wire cout;
wire [3:0] sum;
wire v;
wire [4:0] totalsum;
assign totalsum = {cout,sum};
Add_Sub AS1 (.x(x),.y(y),.cin(cin),.cout(cout),.sum(sum),.v(v));

integer i;
integer z;
initial begin
cin = 0;
for(i=-8;i<8;i=i+1)
begin
    x=i;
    for(z=-8;z<8;z=z+1)
    begin
        y=z;
        #10;
    end
end


cin=1;
for(i=-8;i<8;i=i+1)
begin
    x=i;
    for(z=-8;z<8;z=z+1)
    begin
        y=z;
        #10;
    end
end

$finish;
end
endmodule

```


Simulation results of Add_Sub:






General Look to Add-Sub simulation:

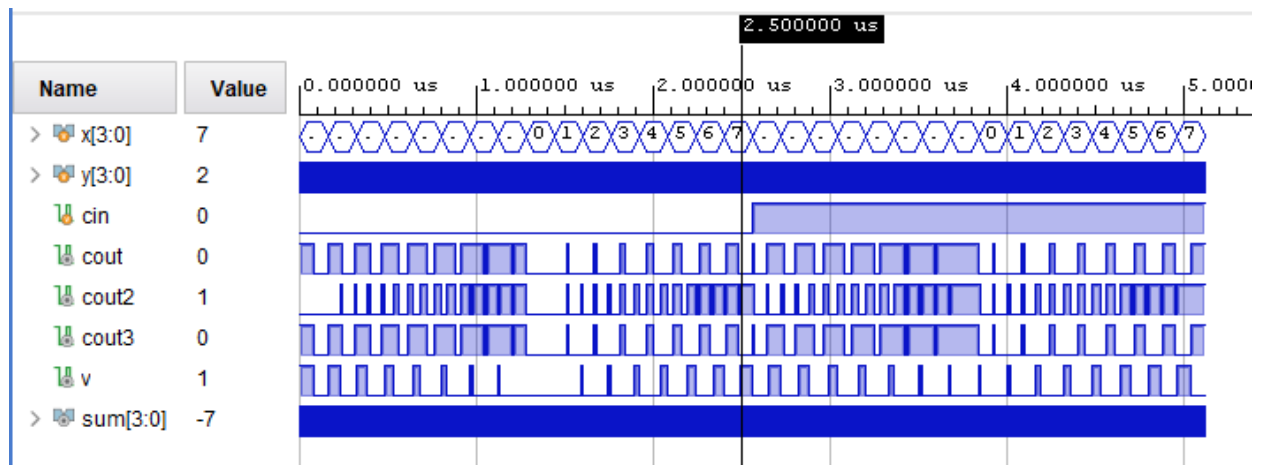


Specific Looks to Add-Sub simulation:

cin=0

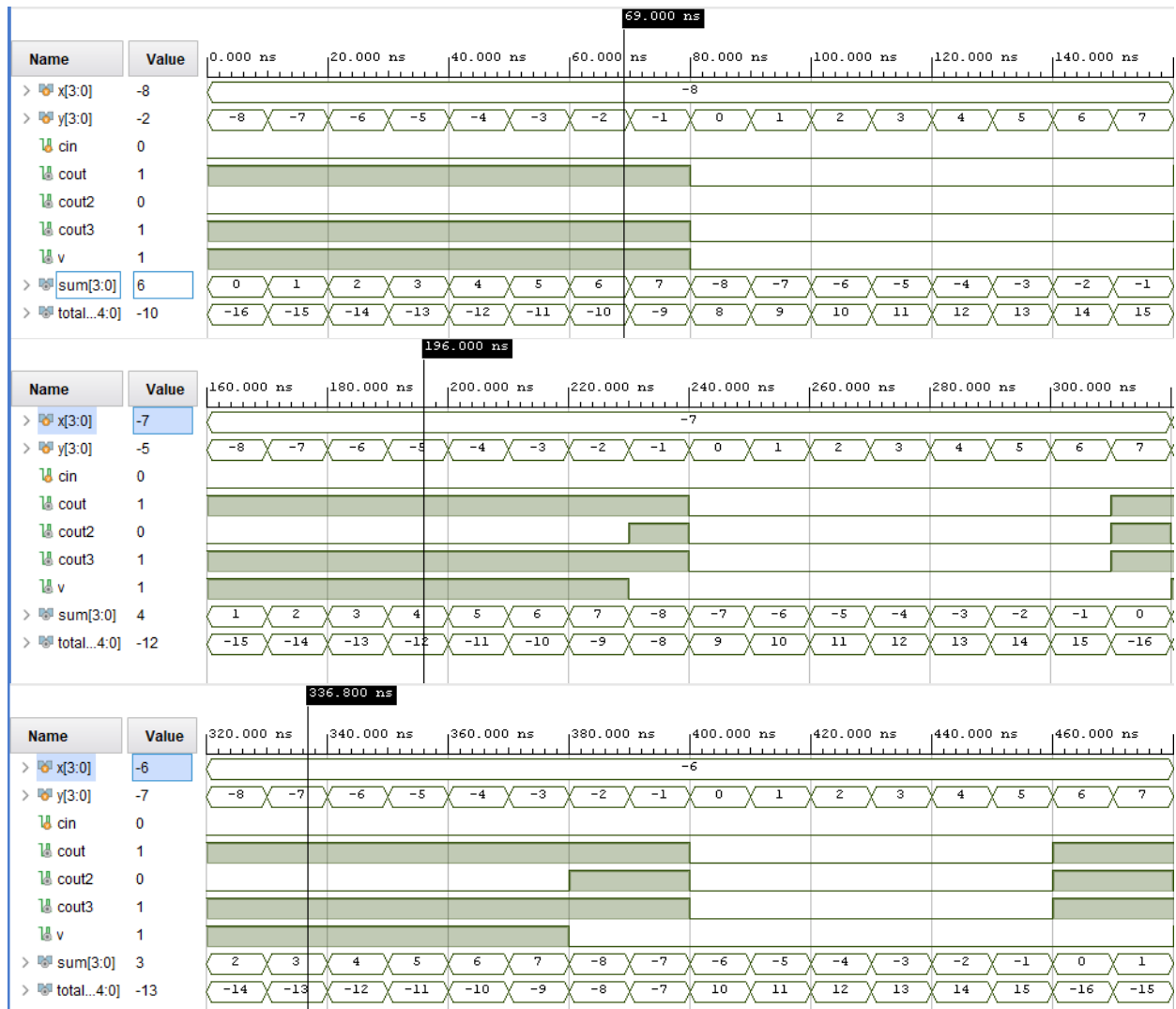


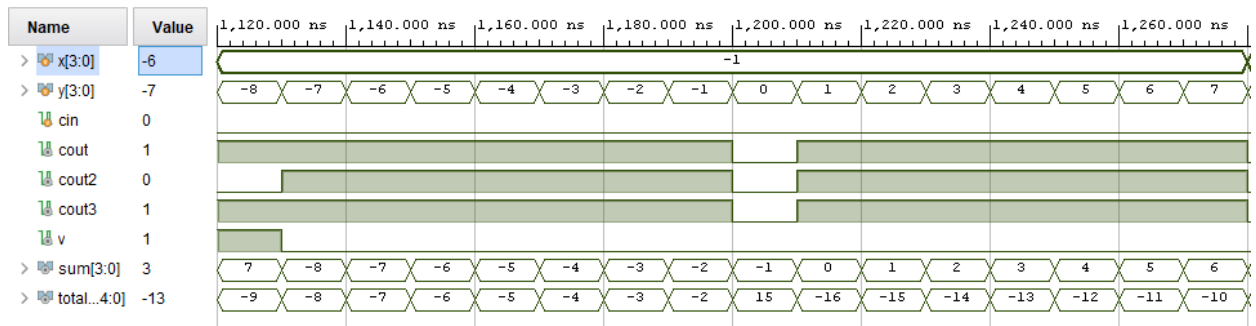
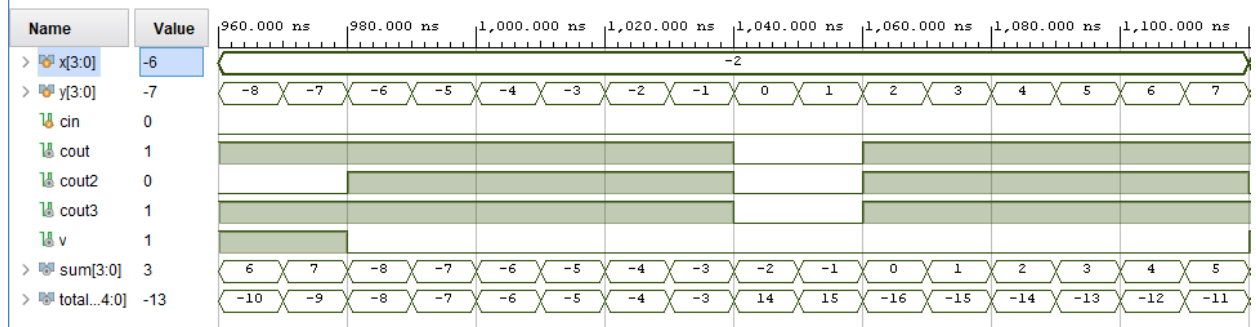
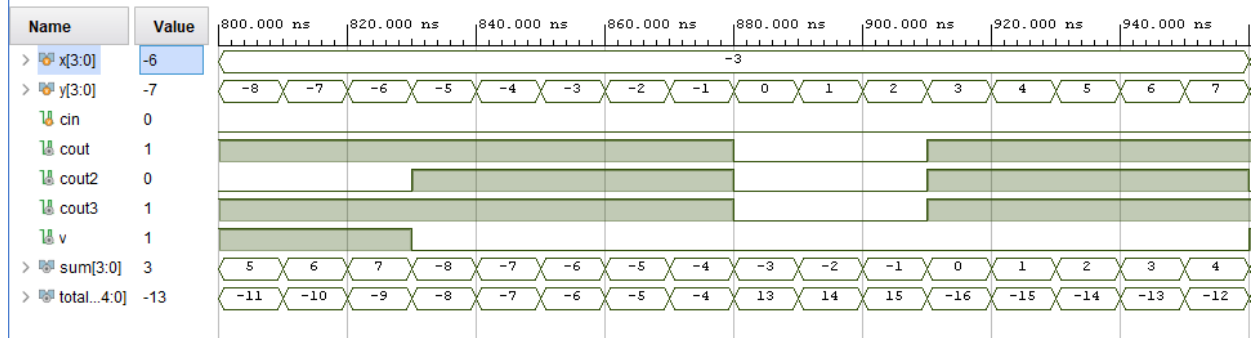
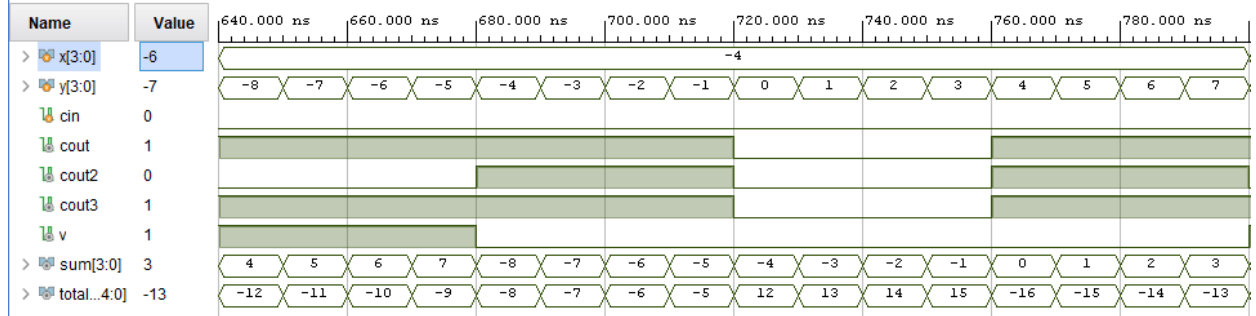
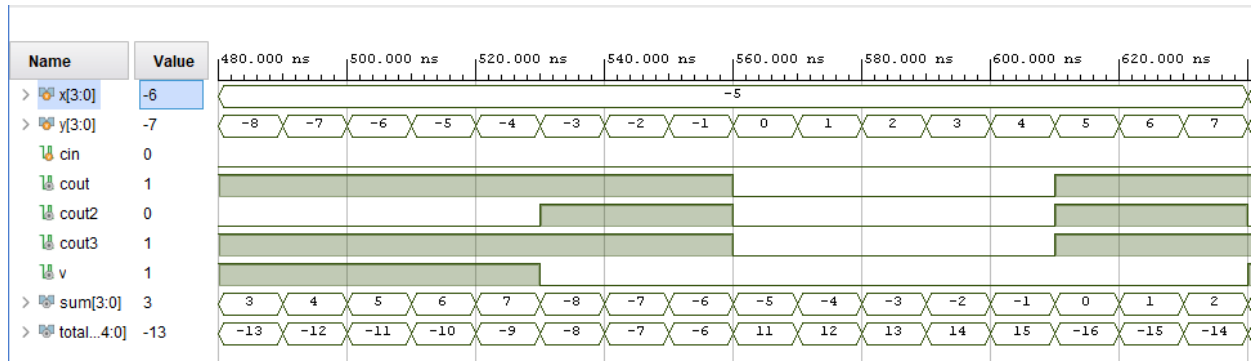





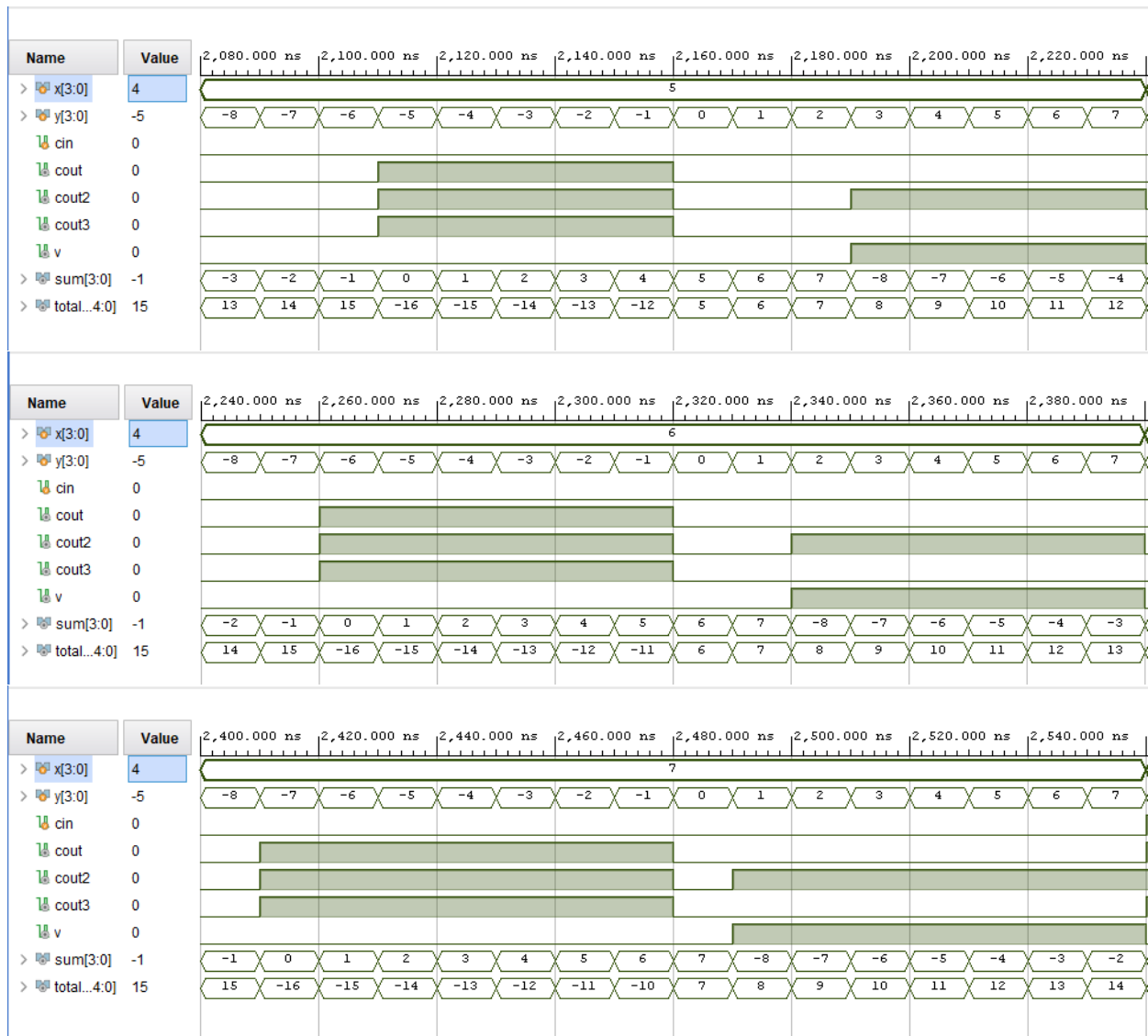


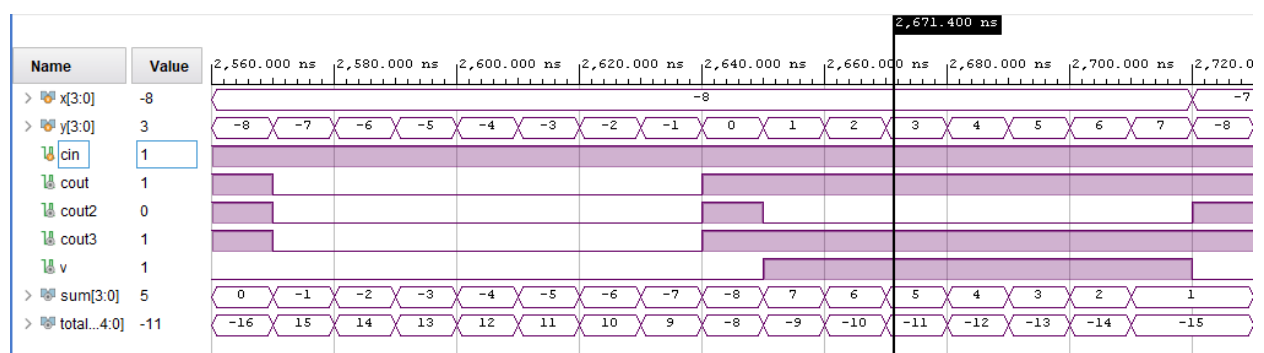Now Cin=1 so i changed colors to read should realize something changed.




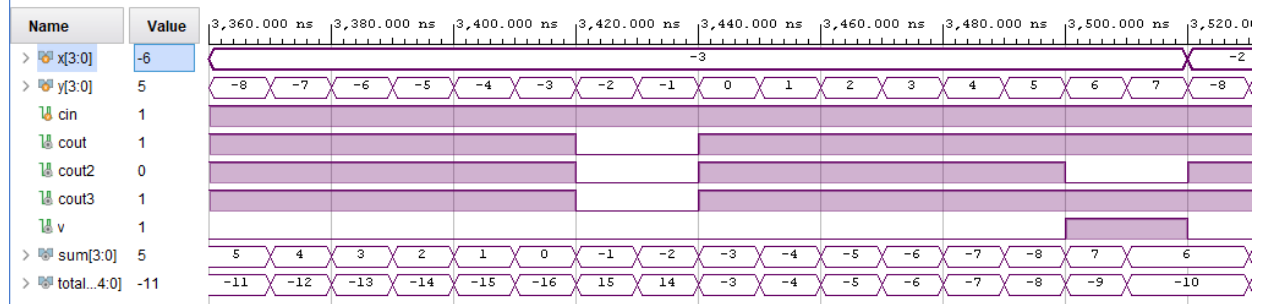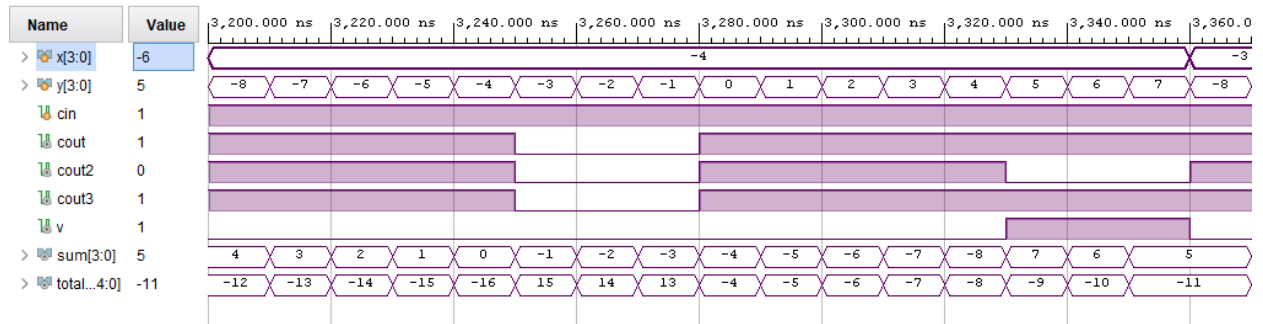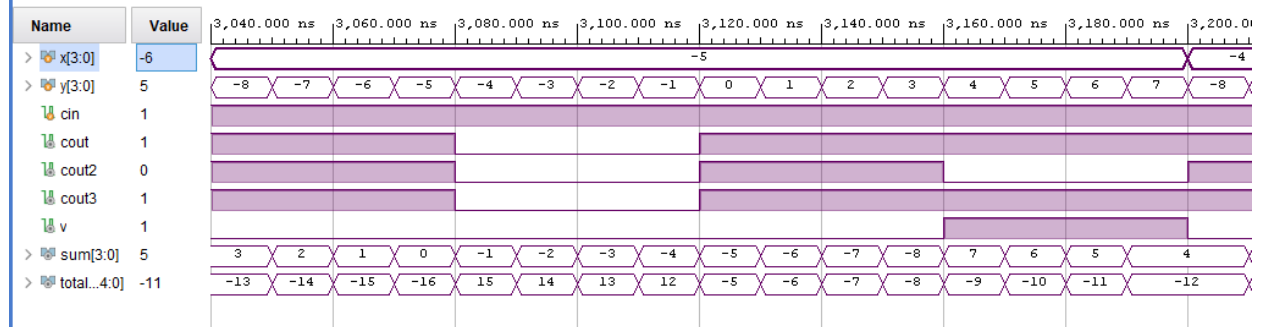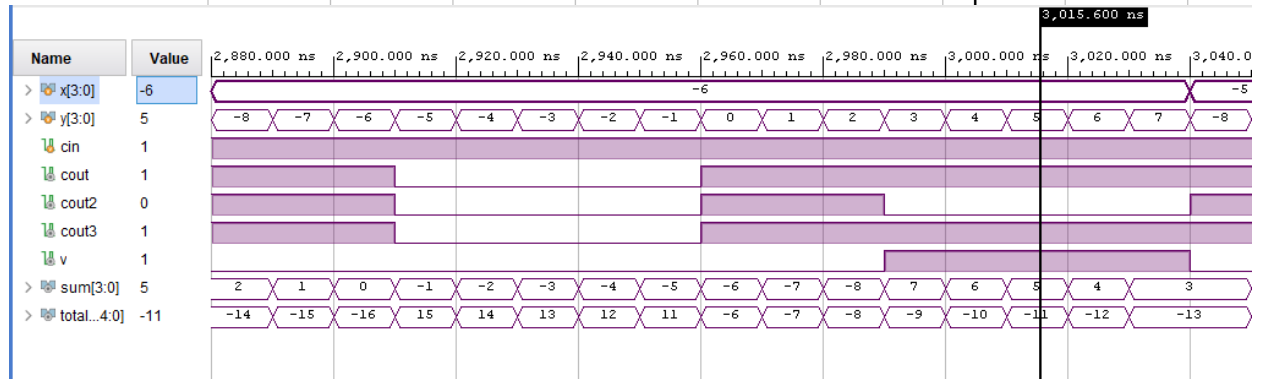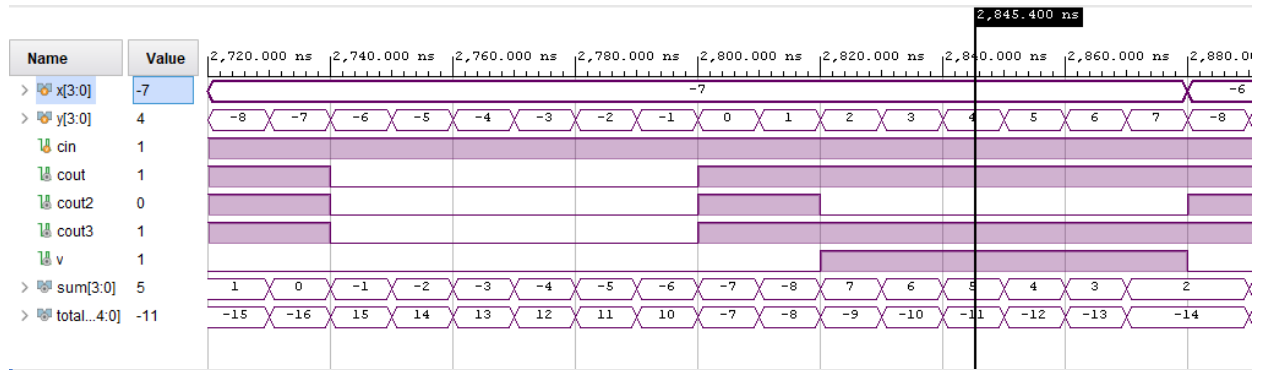

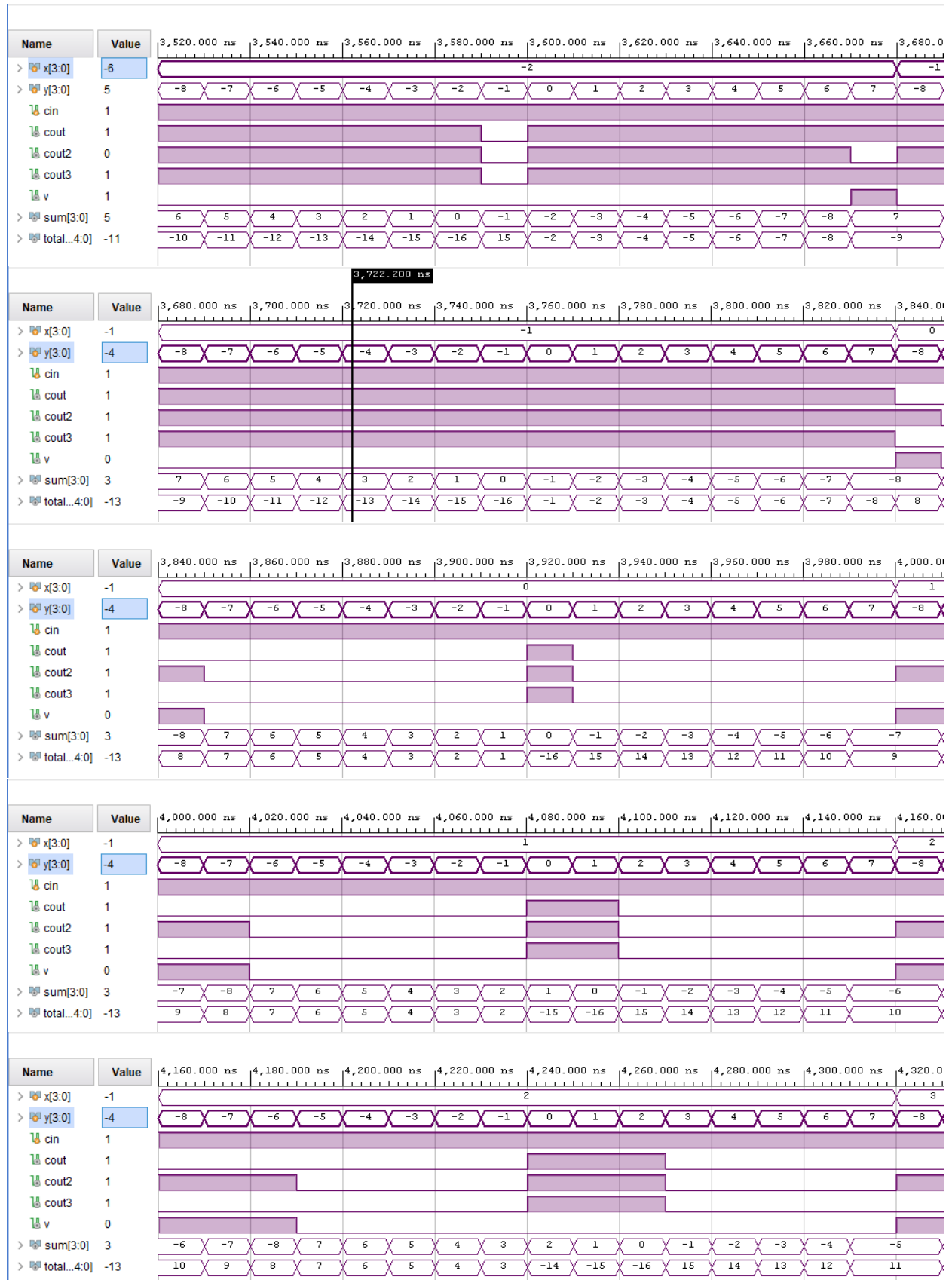


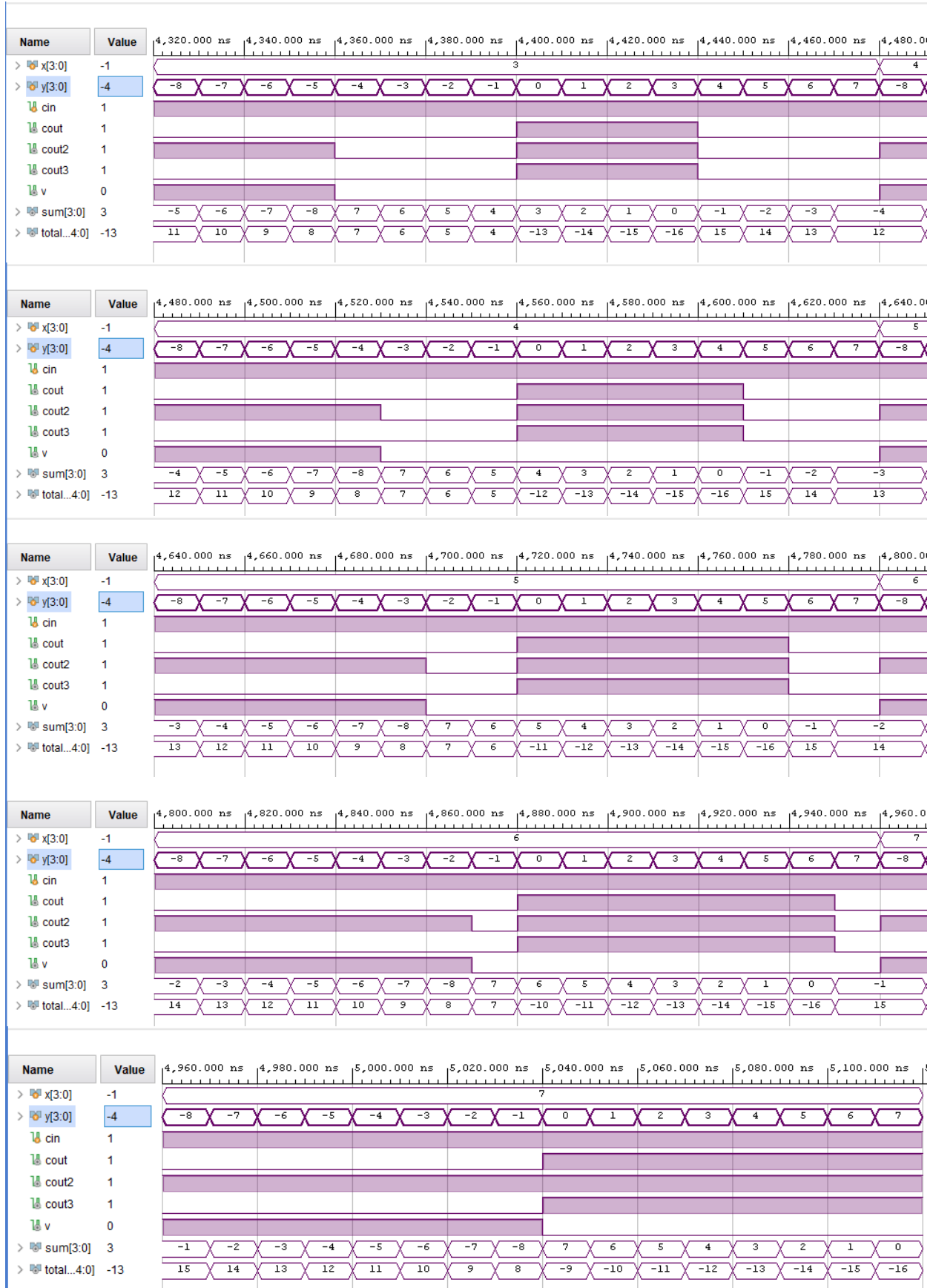

RTL Schematic of Add_Sub:

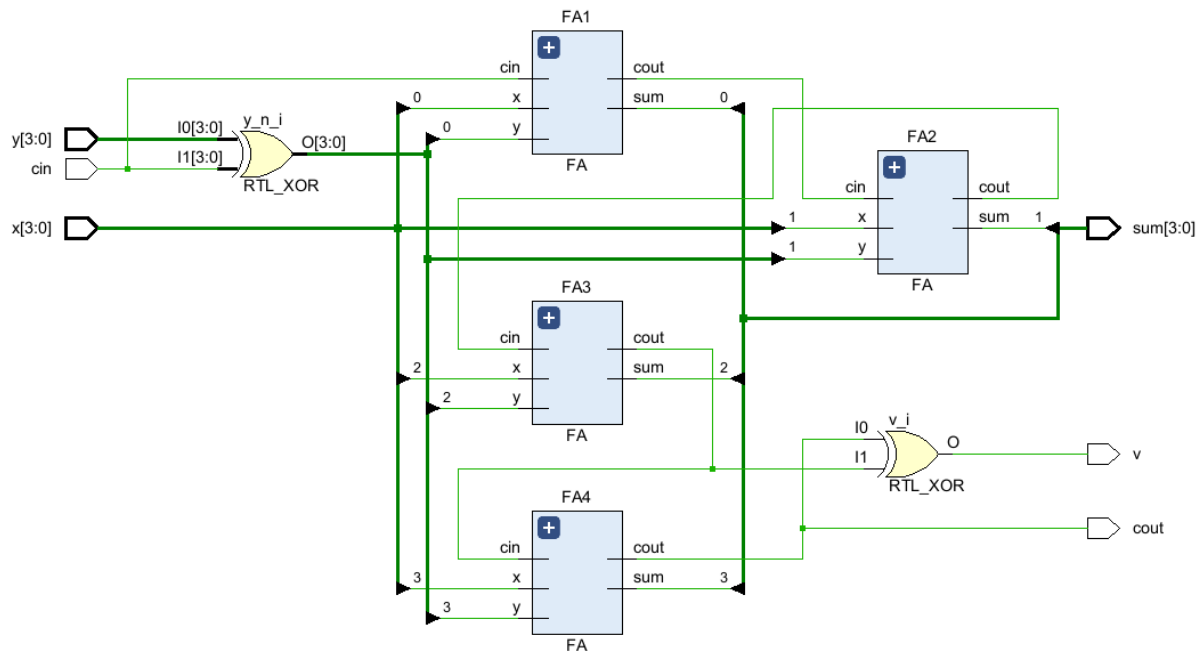


Technology Schematic of Add_Sub:

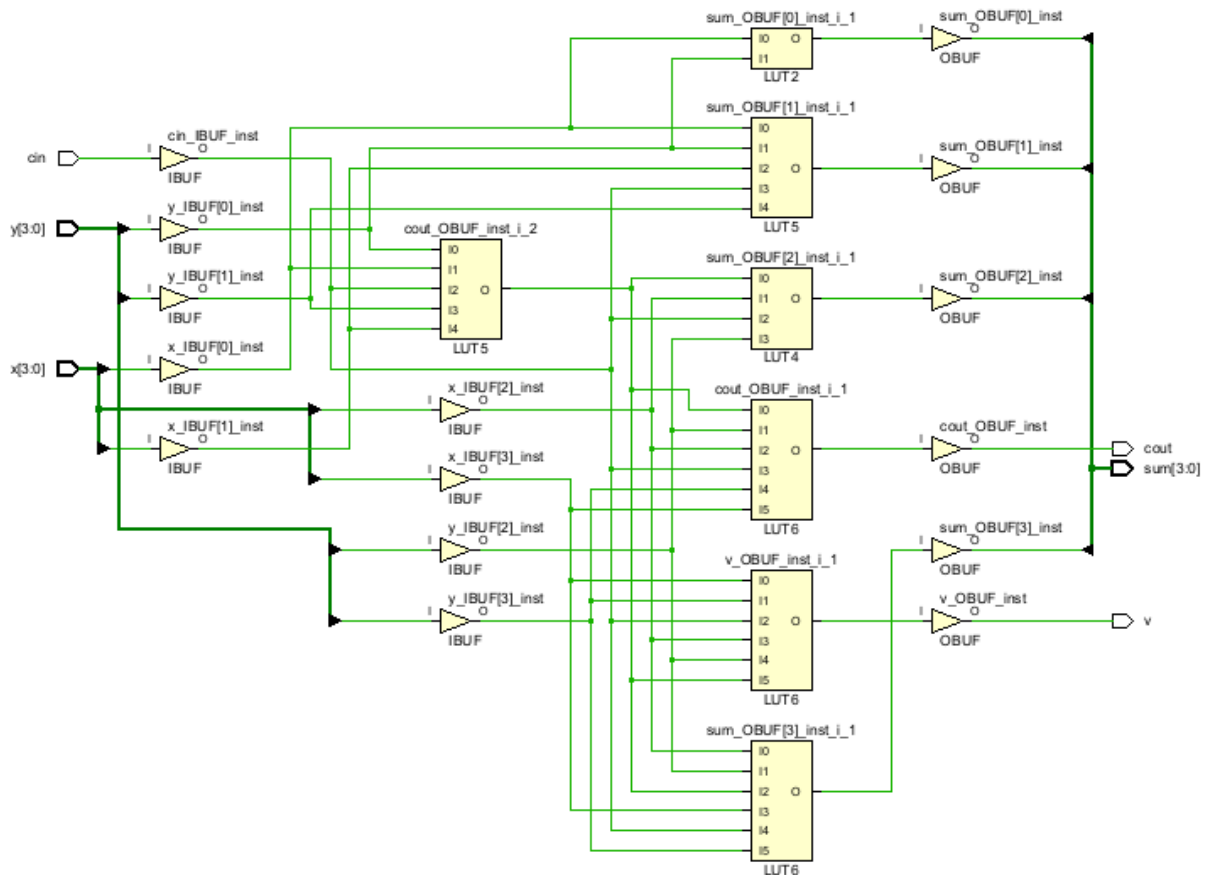

Utilization Report:

Summary

| Resource | Utilization | Available | Utilization % |
|----------|-------------|-----------|---------------|
| LUT | 6 | 32600 | 0.02 |
| IO | 15 | 210 | 7.14 |

 

Timing Summary:

| From Port | To Port | Max Delay | Max Process Corner | Min Delay | Min Process Corner |
|--|--|-----------|--------------------|-----------|--------------------|
| <input checked="" type="checkbox"/> cin | <input checked="" type="checkbox"/> cout | 11.828 | SLOW | 3.742 | FAST |
| <input checked="" type="checkbox"/> x[0] | <input checked="" type="checkbox"/> cout | 9.421 | SLOW | 2.868 | FAST |
| <input checked="" type="checkbox"/> x[1] | <input checked="" type="checkbox"/> cout | 9.278 | SLOW | 2.788 | FAST |
| <input checked="" type="checkbox"/> x[2] | <input checked="" type="checkbox"/> cout | 8.225 | SLOW | 2.392 | FAST |
| <input checked="" type="checkbox"/> x[3] | <input checked="" type="checkbox"/> cout | 8.320 | SLOW | 2.472 | FAST |
| <input checked="" type="checkbox"/> y[0] | <input checked="" type="checkbox"/> cout | 9.448 | SLOW | 2.865 | FAST |
| <input checked="" type="checkbox"/> y[1] | <input checked="" type="checkbox"/> cout | 8.840 | SLOW | 2.653 | FAST |
| <input checked="" type="checkbox"/> y[2] | <input checked="" type="checkbox"/> cout | 8.445 | SLOW | 2.559 | FAST |
| <input checked="" type="checkbox"/> y[3] | <input checked="" type="checkbox"/> cout | 8.057 | SLOW | 2.362 | FAST |
| <input checked="" type="checkbox"/> x[0] | <input checked="" type="checkbox"/> sum[0] | 8.870 | SLOW | 2.694 | FAST |

in CLA

x[3] to cout delay is = 8.818 ns

y[3] to cout delay is = 8.582 ns

in RCA

x[3] to cout delay is = 10.4 ns

y[3] to cout delay is = 10.123 ns

in Add_Subb_with_V

x[3] to cout delay is = 8.328

y[3] to cout delay is = 8.057